

M	T	W	T	F	S	S
			1	2	3	4
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30	31	

Feed Back Amplifier

WK 07 - 07318

FRIDAY


2018 FEBRUARY

16

A feedback amplifier is one in which a fraction of output energy (voltage or current) is fed back to the input by any mean. There are two basic types of feed back in amplifiers

- ① positive feed back
- ② Negative feed back

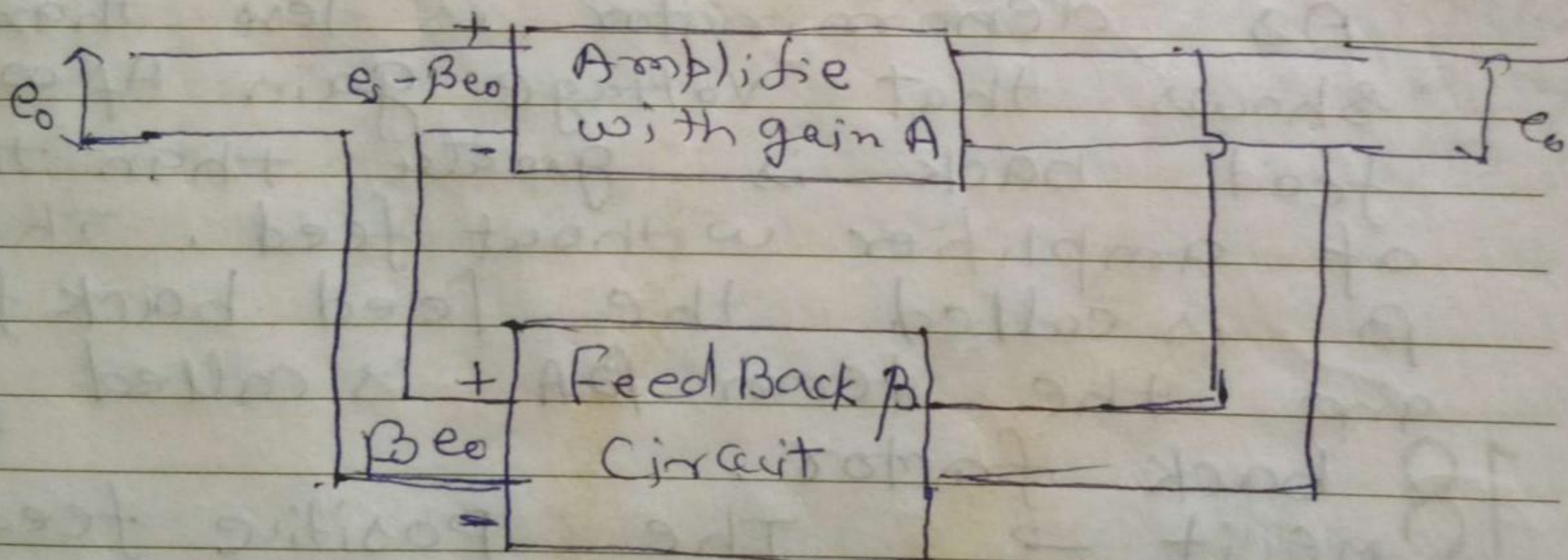positive feed back → when the feed back energy (voltage or current) is in phase with the input signal and thus aids it, the feed back is said to be positive or regenerative.



Let e_i be the input signal voltage and e_o the output voltage

Let B fraction of the output voltage e_o be fed back to the input in the same phase, then the actual input to the amplifier is $e_i + Be_o$. This input is amplified by the gain A of the amplifier.

	S	M	T	W	T	F	S
JAN 2018		1	2	3	4	5	6
	7	8	9	10	11	12	13
	14	15	16	17	18	19	20
	21	22	23	24	25	26	27
	28	29	30				

Voltage e_o

$$e_o = (e_s + \beta e_o) A$$

$$e_o = e_s A + \beta e_o A$$

$$e_o (1 - \beta A) = e_s A$$

∴ Gain of amplifier with positive feed back

$$A_f = \frac{e_o}{e_s} = \frac{A}{1 - \beta A}$$

$$A_f = \frac{A}{1 - \beta A}$$

As denominator is less than unity shows that voltage gain A_f with positive feed back is greater than the gain A of amplifier without feed. The fraction β is called the feed back fraction and the term βA is called feed back factor.

→ The positive feed back increases the gain of the amplifier but it increases the distortion by the same factor. If the positive feed back is sufficiently large, it leads to oscillations, thus making the amplifier unstable.

M	T	W	T	F	S	S
			1	2	3	4
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30	31	


MAR 2018

MONDAY
FEBRUARY

19

Negative feed back

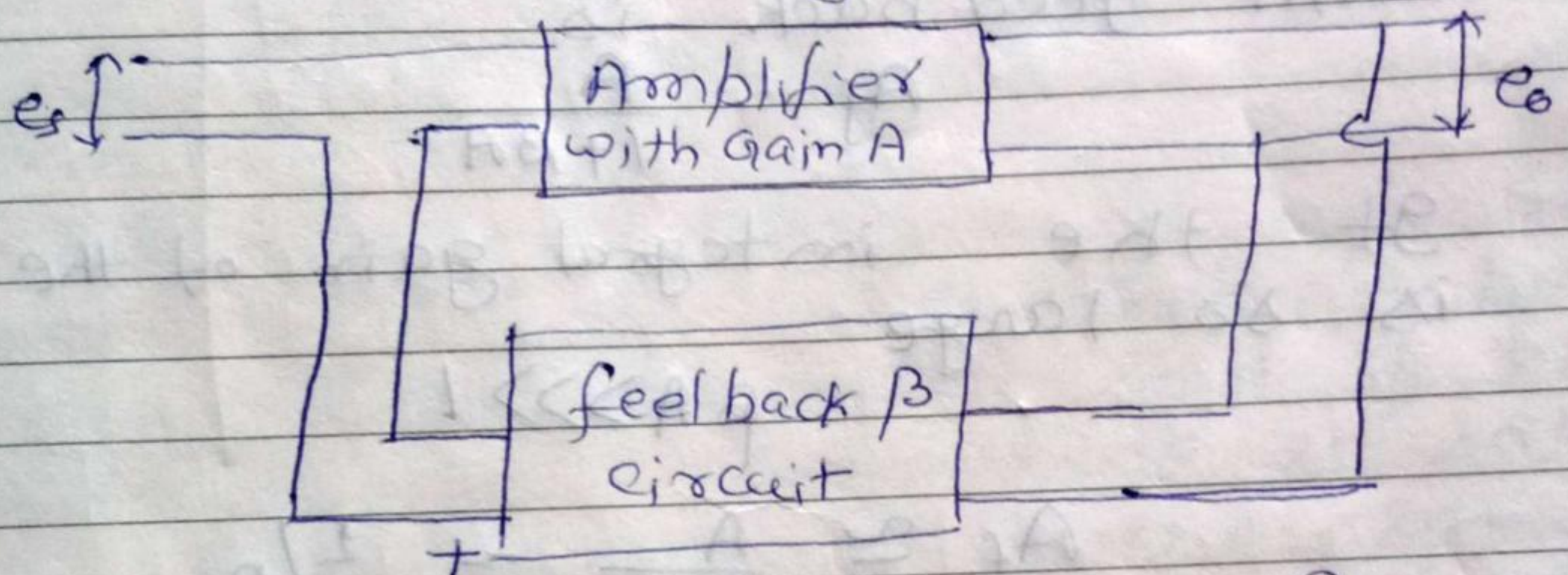when the feed back energy (voltage & current) is feed back in the opposite phase with the input signal and thus opposes it, The feedback is said to be Negative or degenerative.



The feedback factor βe_o and input signal e_s are out of phase. The net input voltage is $(e_s - \beta e_o)$. This input amplified by the gain A of the amplifier must be equal to the output voltage e_o . Thus

$$e_o = (e_s - \beta e_o) A$$

$$A_f = \frac{e_o}{e_s} = \frac{A}{1 + \beta A}$$

The denominator is now greater than unity. Hence the voltage gain A_f with negative feedback is less than the gain A without feedback. The greater is the feedback factor βA , smaller is the gain but at the same time smaller is the distortion.

	S	M	T	W	T	F
JAN 2018	7	1	2	3	4	5
	14	8	9	10	11	12
	21	15	16	17	18	19
	28	22	23	24	25	26

Advantages of Negative feedback

(i) Negative feedback increases the stability of gain of Amplifier →

The gain of the amplifier with feedback is

$$A_f = \frac{A}{1 + \beta A}$$

If the integral gain of the Amplifier is so large

$$\beta A \gg \gg 1$$

$$A_f \approx \frac{A}{\beta A} = \frac{1}{\beta}$$

The gain of the amplifier depends on the properties of the negative feedback. The feedback circuit consists of stable elements like resistors and capacitors, therefore with negative feedback gain does not change with transistor parameters.

(ii) Negative feedback reduces non-linear distortion → The non-linear distortion arises due to curvature of output characteristics of the transistor. A large input signal has a non-linear distortion because its gain changes at various points of the cycle. The negative feedback reduces the

linear distortion in signal amplifiers.

let e_1 & e_n be the amplitudes of first and n th harmonic in the output voltage without feed back, then fractional n th harmonic distortion is

$$D_n = e_n / e_1$$

If a fraction β of output voltage is fed back into input voltage out of phase and if the applied signal amplitude is so adjusted that the output has the same fundamental component e_1' as before then if e_n' is the amplitude of n th harmonic βe_n will appear into the input 180° out of phase with the applied signal and will be amplified by the amplifier to a value $A\beta e_n$ in opposite phase with initial n th harmonic e_n then

$$e_n' = e_n - A\beta e_n$$

$$\frac{e_n'}{e_n} = \frac{1}{1 + A\beta}$$

$$\frac{e_n'}{e_n} = \frac{e_n' / e_1}{e_n / e_1} = \frac{D_n'}{D_n} = \frac{1}{1 + A\beta}$$

Therefore the application of negative feedback reduces non linear distortion

22

THURSDAY


FEBRUARY

2018

	S	M	T	W	T	F	S
JAN 2018	7	8	9	10	11	12	13
	14	15	16	17	18	19	20
	21	22	23	24	25	26	27
	28	29	30	31			

Negative feedback reduces frequency distortion

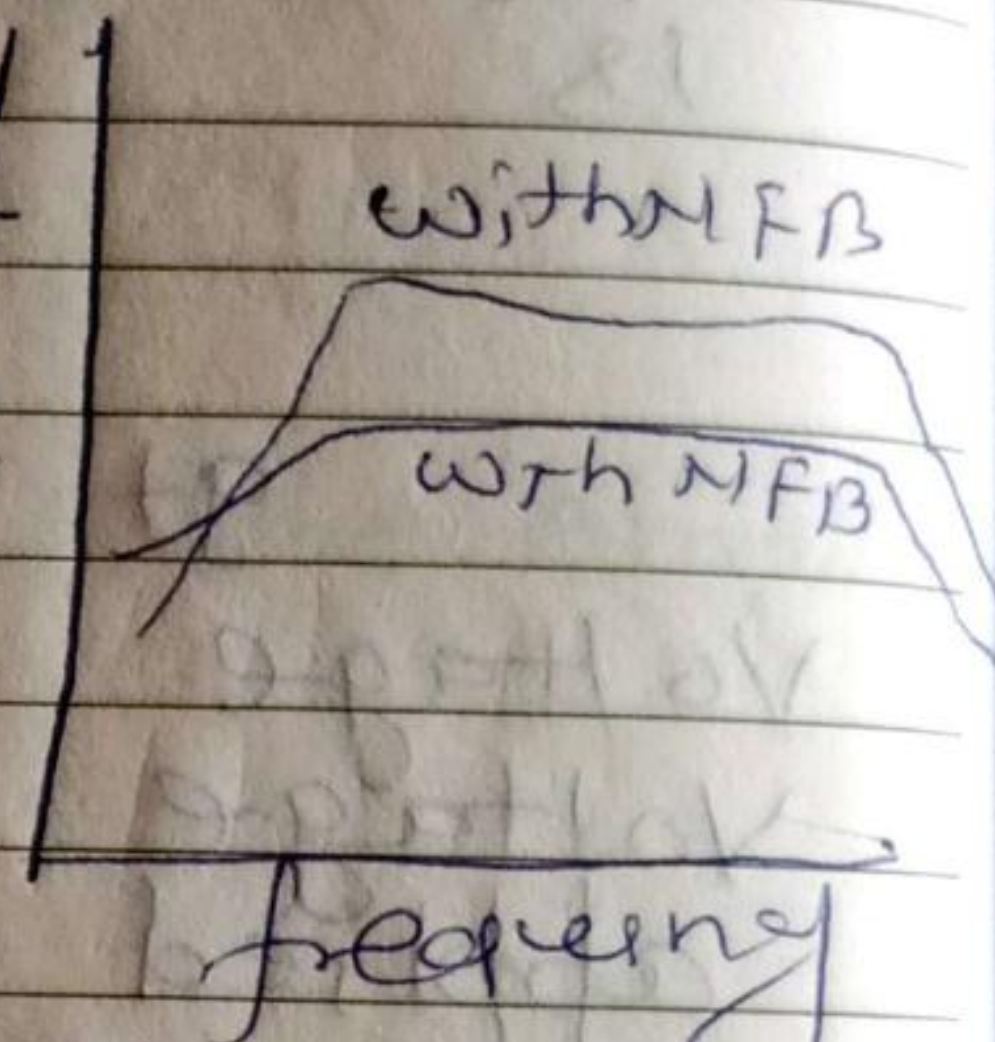This distortion is due to the variation in the gain of an amplifier with frequency. If $AB \gg 1$, $A_f \approx 1/B$. β is independent of frequency then overall gain becomes independent of frequency over the gain range of frequencies for which this condition is satisfied.



IV Negative feedback reduces phase distortion \rightarrow

Negative feedback reduces the phase-shift through an amplifier.

$$\text{Let } A = |A| \angle \theta$$

Then the gain A_f with feedback

$$A_f = |A_f| \angle \theta_f = \frac{A}{1 + \beta A}$$

$$= \frac{|A| \angle \theta}{1 + \beta |A| \cos \theta + j \beta |A| \sin \theta}$$

$$\text{Hence } \theta_f = \theta - \tan^{-1} \frac{\beta |A| \sin \theta}{1 + \beta |A| \cos \theta}$$

Thus by the application of Negative feedback, the phase-shift is reduced by the angle $\tan^{-1} (\beta |A| \sin \theta) / (1 + \beta |A| \cos \theta)$.

M	T	W	T	F	S	S
			1	2	3	4
			8	9	10	11
5	6	7	14	15	16	17
12	13	14	21	22	23	24
19	20	21	28	29	30	31
26	27	28				

Negative feedback
the Input Impedance →

let e_s be the input signal and Z_i the input impedance without feed back. If I_i is the current flowing in the input circuit with negative feed back then input impedance with feed back

$$Z_{if} = e_s / I_i$$

If e_o is the output voltage when negative feedback is applied, then the feedback voltage is βe_o and therefore, the net input voltage with negative feedback is $(e_s - \beta e_o)$

$$I_i = \frac{e_s - \beta e_o}{Z_i}$$

gain Amplifier $A = \frac{e_o}{e_s - \beta e_o}$

$$e_o = \frac{A e_s}{1 + \beta A}$$

$$I_i = \left(e_s - \frac{\beta A e_s}{1 + \beta A} \right) \cdot \frac{1}{Z_i}$$

$$= e_s \left(\frac{1 + \beta A - \beta A}{1 + \beta A} \right) \cdot \frac{1}{Z_i}$$

$$I_i = e_s \left(\frac{1}{1 + \beta A} \right) \cdot \frac{1}{Z_i}$$

$$Z_{if} = e_s / I_i = Z_i (1 + \beta A) \quad \left[\frac{Z_{if}}{Z_i} = 1 + \beta A \right]$$

4 SATURDAY
15 FEBRUARY 2018

negative feedback reduces the output Impedance →
 let e_s be the input signal and i_i the input impedance without feedback. If i_i is the current flowing in the input circuit with negative feedback
 input Impedance with feedback

$$Z_{if} = e_s / i_i$$

If e_o is the output voltage when negative feedback is applied, then the feedback voltage is βe_o .
 The net input voltage with negative feedback ($e_s - \beta e_o$)

$$\therefore i_i = \frac{e_s - \beta e_o}{Z_i}$$

Gain Amplifier $A = \frac{e_o}{e_s - \beta e_o}$

$$e_o = \frac{A e_s}{1 + \beta A}$$

25

SUNDAY

$$i_i = \left(e_s - \frac{\beta A e_s}{1 + \beta A} \right) \cdot \frac{1}{Z_i}$$

$$= e_s \left(\frac{1}{1 + \beta A} \right) \cdot \frac{1}{Z_i}$$

$$e_s / i_i = Z_i \cdot (1 + \beta A)$$

output Impedance $Z_{of} = Z_o / (1 + \beta A)$